

GATE

January 18, 2024

1. A counter is constructed with three D flip-flops. The input-output pairs are named (D_0, Q_0) , (D_1, Q_1) , and (D_2, Q_2) , where the subscript 0 denotes the least significant bit. The output sequence is desired to be the Gray-code sequence 000, 001, 011, 010, 110, 111, 101, and 100, repeating periodically. Note that the bits are listed in the $Q_2 Q_1 Q_0$ format. The combinational logic expression for D_1 is (GATE-EE2021,37)

- (a) $Q_2 Q_1 Q_0$
- (b) $Q_2 Q_0 + Q_1 \bar{Q}_0$
- (c) $\bar{Q}_2 Q_0 + Q_1 \bar{Q}_0$
- (d) $Q_2 Q_1 + \bar{Q}_2 \bar{Q}_1$